


Directions

- Carefully read the overhead projection for any additional directions specific to this quiz/exam.
- In the header, replace the highlighted text with your name and remove the highlight.
- Make your final answers clear, ideally with circles or in green. Correct answers made clear "after the fact" will not be graded.
- Any questions with an answer but no justifying work will be graded as **incorrect**.

All work and answers must be done using a MS Word "drawing".
(Exceptions are made for those with accommodations requests.)

>>>>> ALL TEXT OR OTHER FORMS OF ANSWERS WILL BE IGNORED!!!!!! <<<<<<
>>>>> THIS INCLUDES POWERPOINT AND OTHER VECTORIZED DRAWINGS !!!!! <<<<

- Violating any of these rules or other malicious behavior will result in a 0 grade and disciplinary action report to the provost's office.
- Partial credit is awarded for flawed work or answering the question outside of given constraints: **do not leave an answer blank if you can answer a similar question.**
- Any indication of copied work, especially identical incorrect answers or identically formatted answers will **1)** be marked as incorrect and **2)** be referred to the Provost's Office for academic misconduct.
- Submit your final answers as a **PDF** document by the deadline.

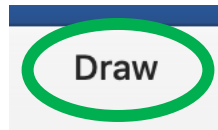

	Expression	Dual
P2	$a + 0 = a$	$a \cdot 1 = a$
P3	$a + b = b + a$	$ab = ba$
P4	$a + (b + c) = (a + b) + c$	$a(bc) = (ab)c$
P5	$a + bc = (a + b)(a + c)$	$a(b + c) = ab + ac$
P6	$a + \bar{a} = 1$	$a \cdot \bar{a} = 0$
T1	$a + a = a$	$a \cdot a = a$
T2	$a + 1 = 1$	$a \cdot 0 = 0$
T3	$\bar{\bar{a}} = a$	
T4	$a + ab = a$	$a(a + b) = a$
T5	$a + \bar{a}b = a + b$	$a(\bar{a} + b) = ab$
T6	$ab + a\bar{b} = a$	$(a + b)(a + \bar{b}) = a$
T7	$ab + \bar{a}bc = ab + ac$	$(a + b)(a + \bar{b} + c) = (a + b)(a + c)$
T8	$\overline{a + b} = \bar{a}\bar{b}$	$\overline{ab} = \bar{a} + \bar{b}$
T9	$ab + \bar{a}c + bc = ab + \bar{a}c$	$(a + b)(\bar{a} + c)(b + c) = (a + b)(\bar{a} + c)$
T10(a)	$f(x_1, x_2, \dots, x_n) = x_1 \cdot (f(1, x_2, \dots, x_n) + \bar{x}_1 \cdot f(0, x_2, \dots, x_n))$	
T10(b)	$f(x_1, x_2, \dots, x_n) = [x_1 + f(0, x_2, \dots, x_n)][\bar{x}_1 + f(1, x_2, \dots, x_n)]$	


Haegang Yang

This page is intentionally left blank: you may use it as scratch “paper”.

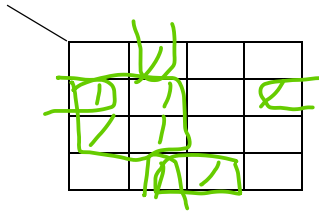Problem 1 (2.5 points)

Minimize the following function using K-maps into its **minimal sum-of-products** form.

$$f(a,b,c,d) = \bar{a}\bar{b}cd + \bar{b}\bar{c}d + ab\bar{c} + \bar{a}b\bar{d} + \bar{a}b\bar{c}d$$





$$\bar{b}\bar{c} + \bar{a}b\bar{d} + \bar{b}\bar{c}d + \bar{a}b\bar{c}d$$

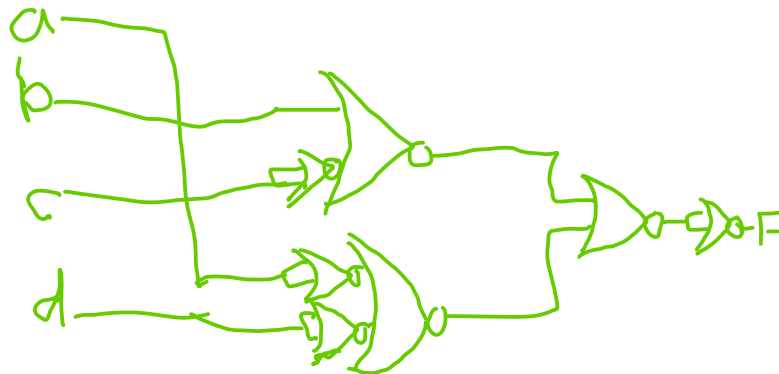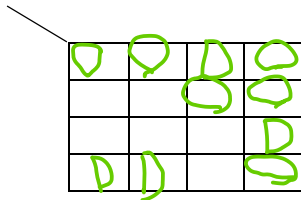Problem 2 (2.5 points)



Make the following function using the minimum number of NOR gates.

$$f(A,B,C,D) = \prod(0,1,2,6,7,10) \cdot D(3,8,9,14)$$



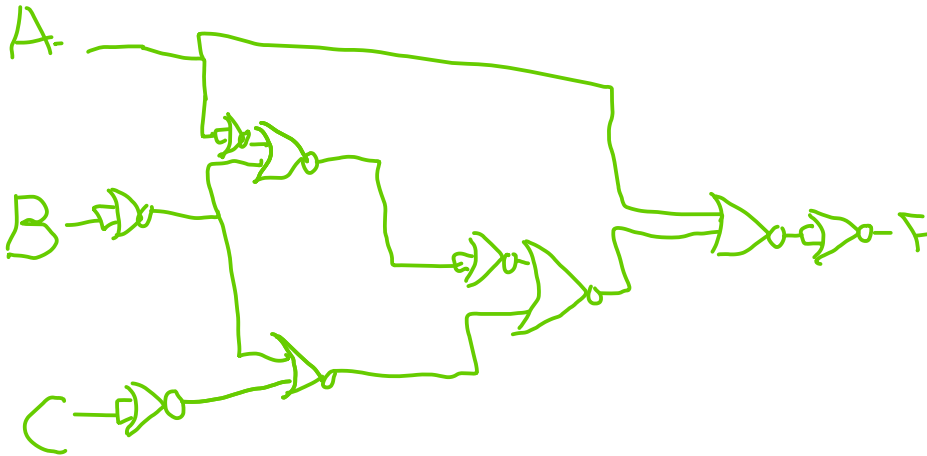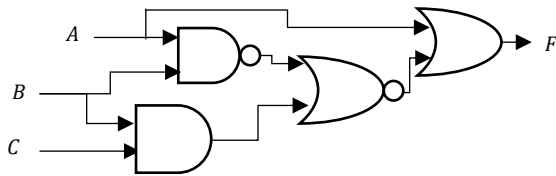
Problem 3 (2.5 points)

Convert the following circuit into one using only NOR gates (and no inverters). Do not optimize the circuit except for the number of "inverters".



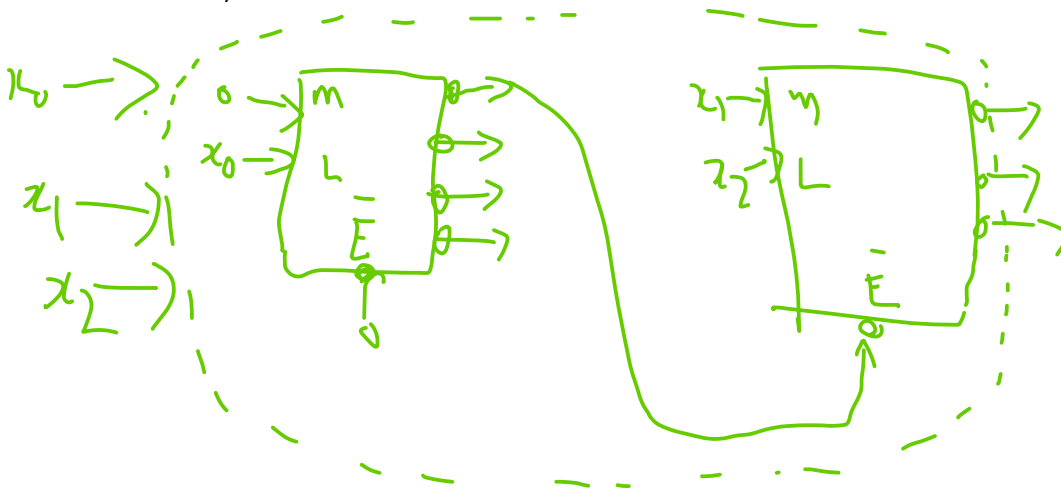
Problem 4 (2.5 points)

Create a 2-to-3 active-low decoder with an active-low enable. Name your inputs $\{x_2, x_1, x_0, \bar{E}\}$ (with x_0 as the LSB).



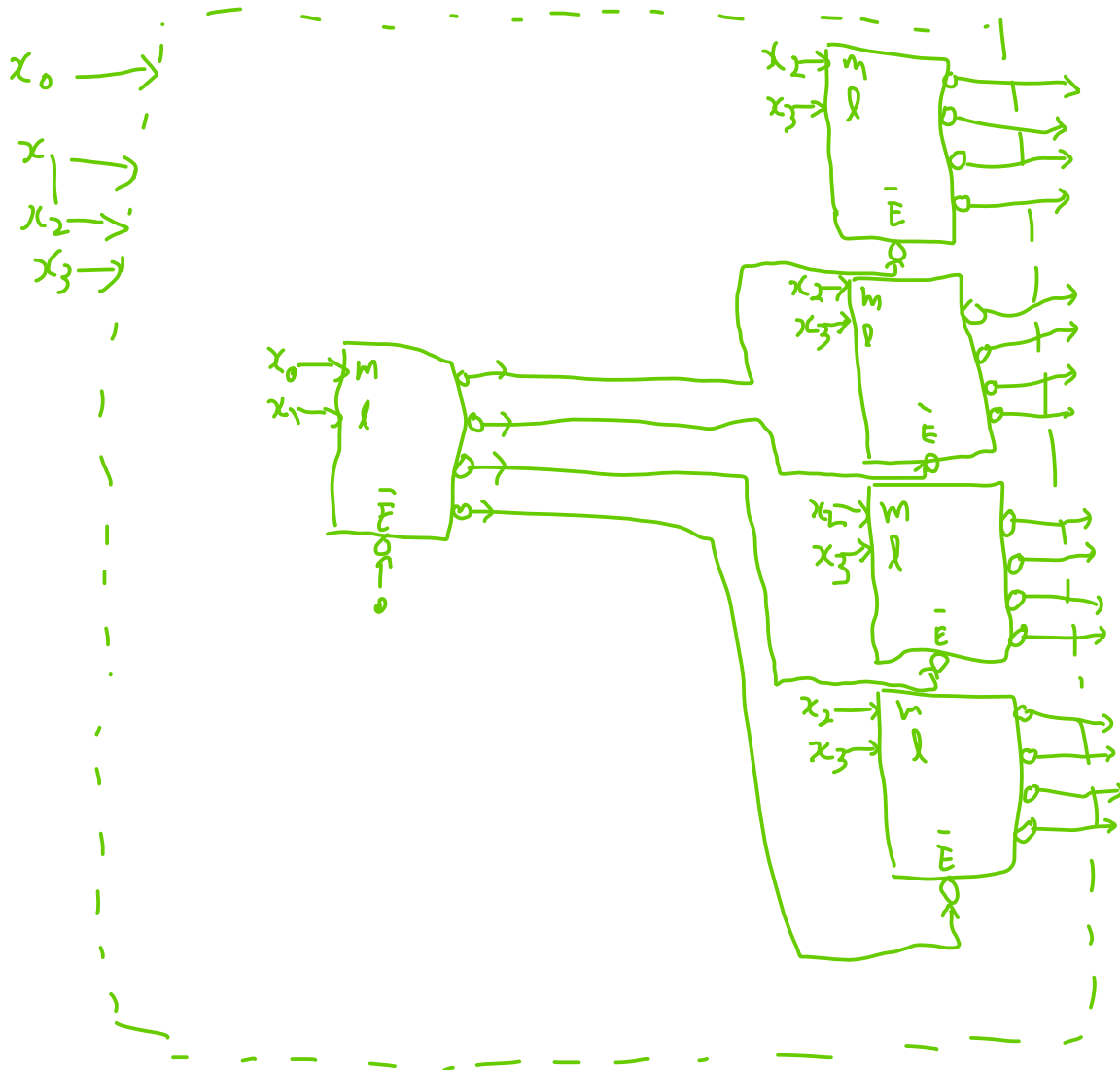
Problem 5 (4 points)

Design a 4-to-16 active-low decoder using only 2-to-4 active-low decoder modules. No other gate types or modules may be used (you may use constant values). Assume that each 2-to-4 decoder has one active-low enable input, \bar{E} . Name your 4-to-16 decoder inputs $\{x_3, x_2, x_1, x_0\}$ with x_3 being the MSB.



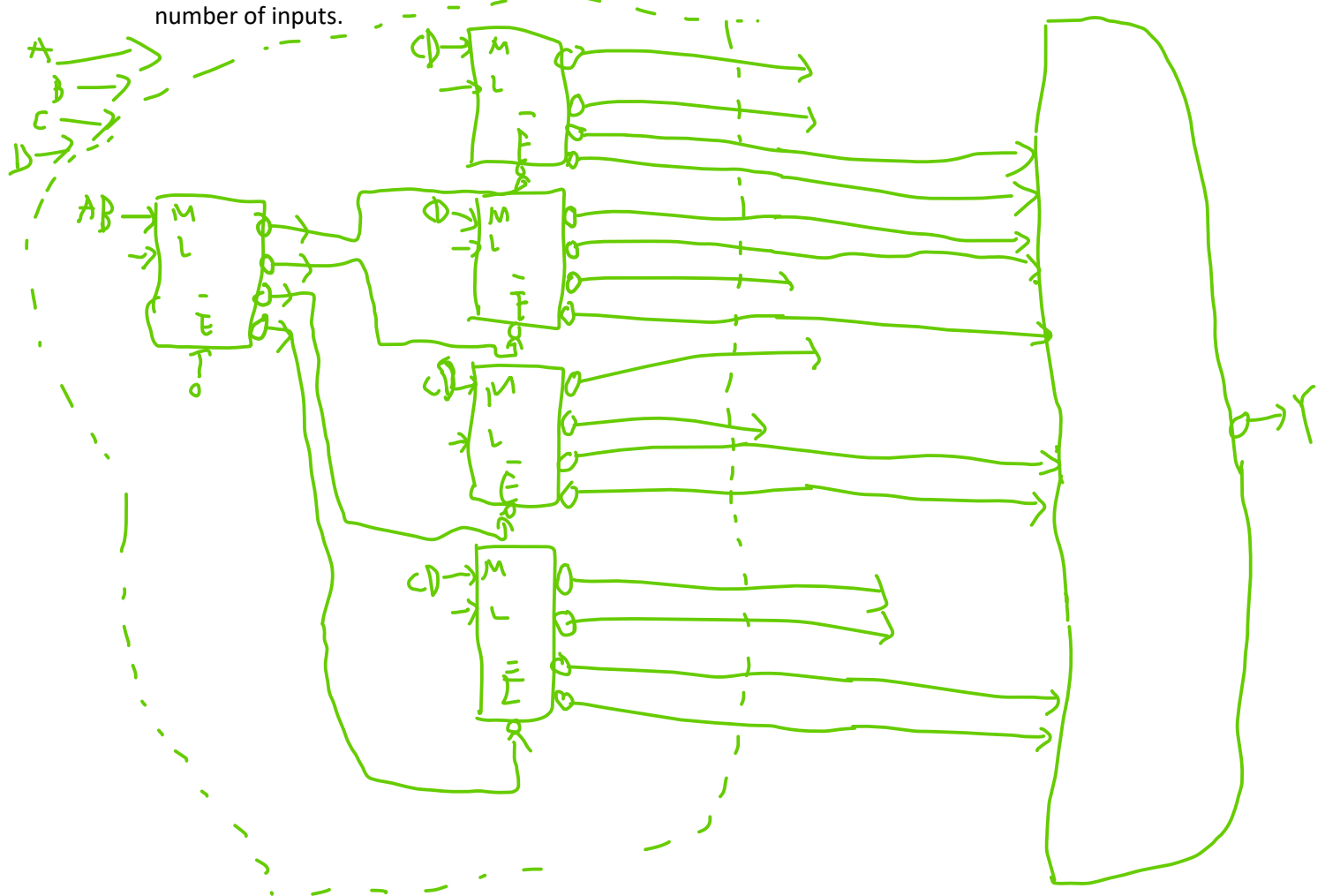
Problem 6 (3 points)

Realize the expression $Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}\bar{B}CD + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + ABC\bar{D} + AB\bar{C}D$ using the following using 2-to-4 active-low decoders (with active-low enables) and a single logic gate of any number of inputs.



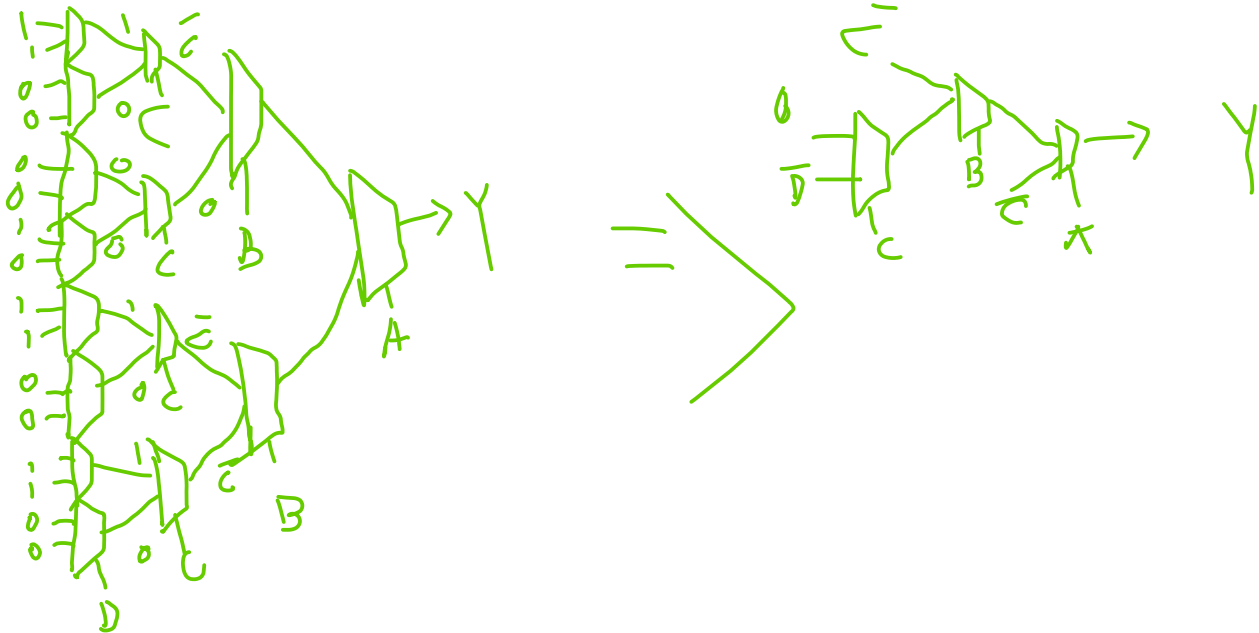Problem 7 (2.5 points)

Realize the expression $Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}BC\bar{D} + \bar{A}\bar{B}CD + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + ABC\bar{D} + ABCD$ using a minimal number of 2-to-1 multiplexers.



Problem 8 (3 points)

Create a 5-bit subtractor using using NAND and XOR gates.

